

Question 3

- a) Given the 2-cube $A = 0x0x$, how many other 2-cubes, B , exist such that $A * B = 0101$?

Answer: ___1 (X1X1)_____

- b) Is the following statement true or false: In an n -variable Boolean space, the number of $(n-1)$ -cubes that exist is equal to $2n$.

Answer: ___True_____

- c) Given the following implicants for a function, f , list the prime implicants.

$$f = \{1xx1x10, 11x0x10, 10x0x10, 111x1x0\}$$

Prime implicants: _____1XXXX10, 111X1X0_____

$$11X0X10 * 10X0X10 = 1XX0X10 \text{ (second and third implicants)}$$

$$1XX1X10 * 1XX0X10 = 1XXXX10 \text{ (first implicant with previous result)}$$

d) Given

$$C^{k+1} = \{0x00, x10x, 11xx, 1000\}$$

$$G^{k+2} = \{0100, x100, x000, 110x, 1x00\}$$

Evaluate the following:

$$C^{k+2} = \{C^{k+1} \cup G^{k+2} - (\text{redundant cubes})\}$$

$$C^{k+2} = \underline{\quad} 0X00, X10X, 11XX, X000, 1X00$$

The redundant cubes are

$$0100 \subset 0X00$$

$$X100 \subset X10X$$


$$1000 \subset 1X00$$

$$110X \subset 11XX$$

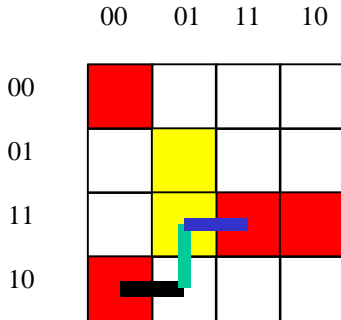
e) The prime implicants for a function f are $\{00X0, 01X1, 011X, 0X10, X111, 1X11\}$. By using a K-map, determine the essential prime implicants for the function

Answer: _____ $00X0, 1X11, 01X1$

Essential prime implicants are shaded. Non essential are outlined as "bars".



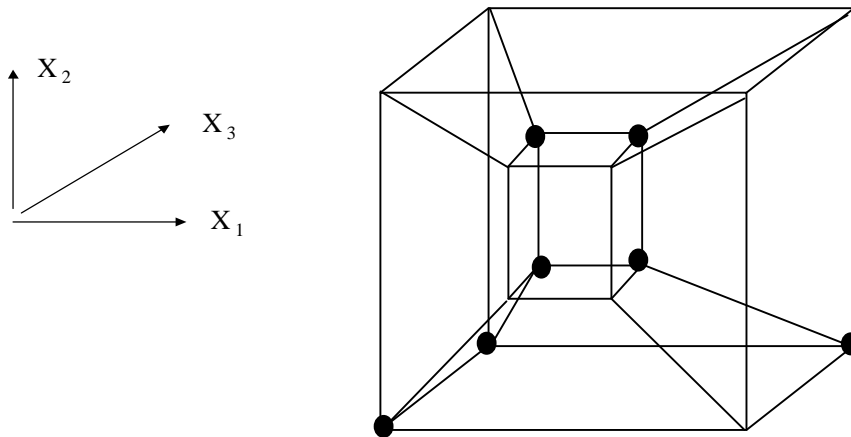f) The figure below represents the Boolean space (x_1, x_2, x_3, x_4) . Coordinates are defined as in class, as indicated below (x_4 is 1 on outer cube):



A function f is represented by the vertices shown in bold

g) Write an expression in cubical representation that represents a minimal sum-of-products implementation:

Answer: _____ $X01X, XX10, 00X1$ _____

h) Consider a 7-variable Boolean space. One vertex in this space is 1111000. If you could draw a figure representing the 7-variable space, which other vertices would be connected to by edges to the vertex 1111000?

Answer: _____ $0111000, 1011000, 1101000, 1110000, 1111100, 1111010, 1111001$

Question 4

Figure 1 shows the array implementation of a 4x4 bit array multiplier.


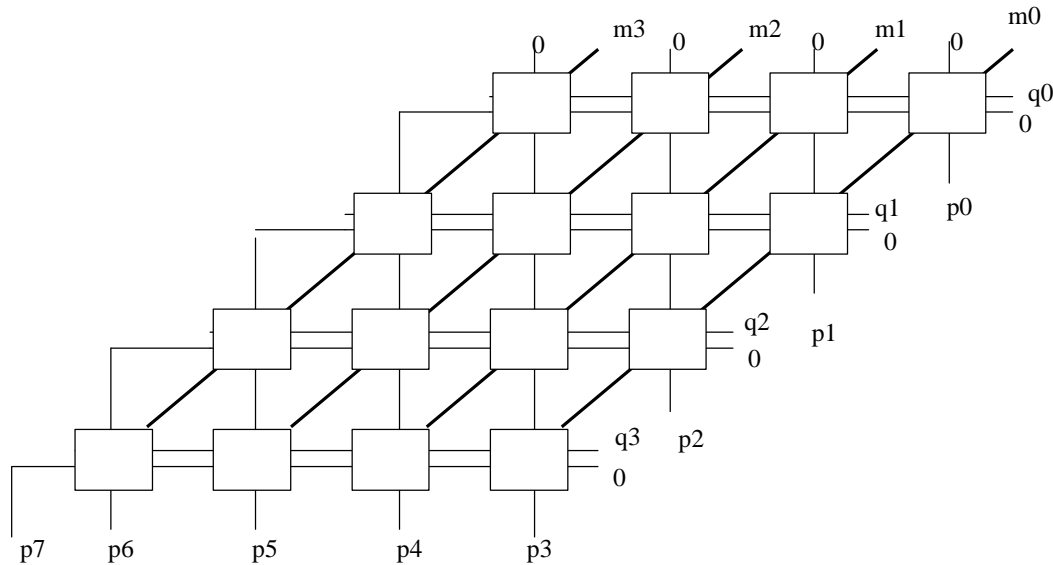


Figure 1 :4x4bit array multiplier

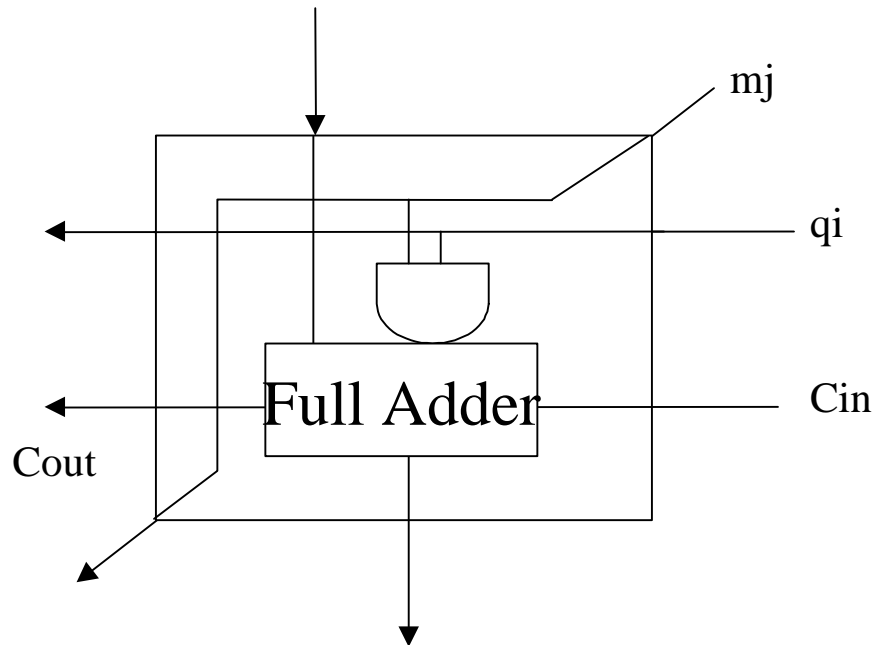a) Draw the internal part of the multiplier cell.



Assume that the different gates have the propagation delays defined below.


- NOT: 0.4 ns
- Nand2: 0.6 ns (2-input Nand gate)
- Xor2 1 ns

Full Adders are implemented according to the following equations

$$s = (a \oplus b) \oplus c_{in}$$

$$c_{out} = ab + c_{in}(a \oplus b)$$

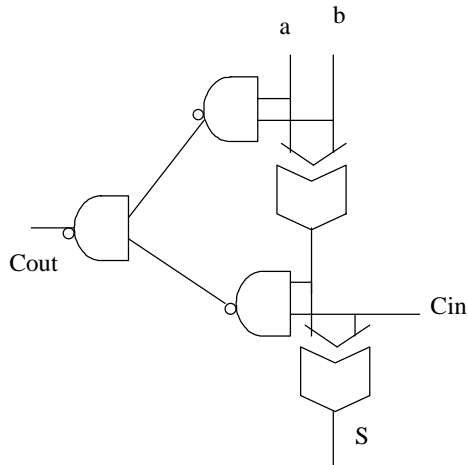b) Draw the Full Adder by using the minimum number of Xor2, Nand2 and NOTgates.



c) What are the propagation delays for the full adder? (Fill up the table below)

| INPUT | | OUTPUT | PROPAGATION DELAY |
|----------|----|-----------|-------------------------------------|
| a or b | TO | S | $2 \times 1 = 2 \text{ ns}$ |
| a or b | TO | C_{out} | $2 \times 0.6 + 1 = 2.2 \text{ ns}$ |
| C_{in} | TO | S | 1 ns |
| C_{in} | TO | C_{out} | $2 \times 0.6 = 1.2 \text{ ns}$ |

d) Compute the worst-case propagation delay (in ns) from input to output for this array multiplier. This forms the *critical path*. Show details of your work and **highlight the critical path** in the figure below.

The propagation delay includes the AND gate m0q0 and one path to reach p6 or p7.
 The propagation delays include

- Horizontal propagation $t_h = 1.2$ ns
- Horizontal to vertical propagation $t_{hv} = 1$ ns
- Vertical propagation $t_v = 2$ ns
- Vertical to horizontal propagation $t_{vh} = 2.2$ ns


As $t_h > t_{hv}$ and $t_{vh} > t_v$, the critical path is for p7 (not p6)

The two “essential” critical paths are

The bold one : $t_{AND} + 2 t_{vh} + 5 t_h + 2 t_v + 1 t_{hv} = 1 + 4.4 + 6 + 4 + 1 = 16.4$ ns

The dash one: $t_{AND} + 4 t_{vh} + 3 t_{hv} + 3 t_h = 1 + 8.8 + 3 + 3.6 = 16.4$ ns

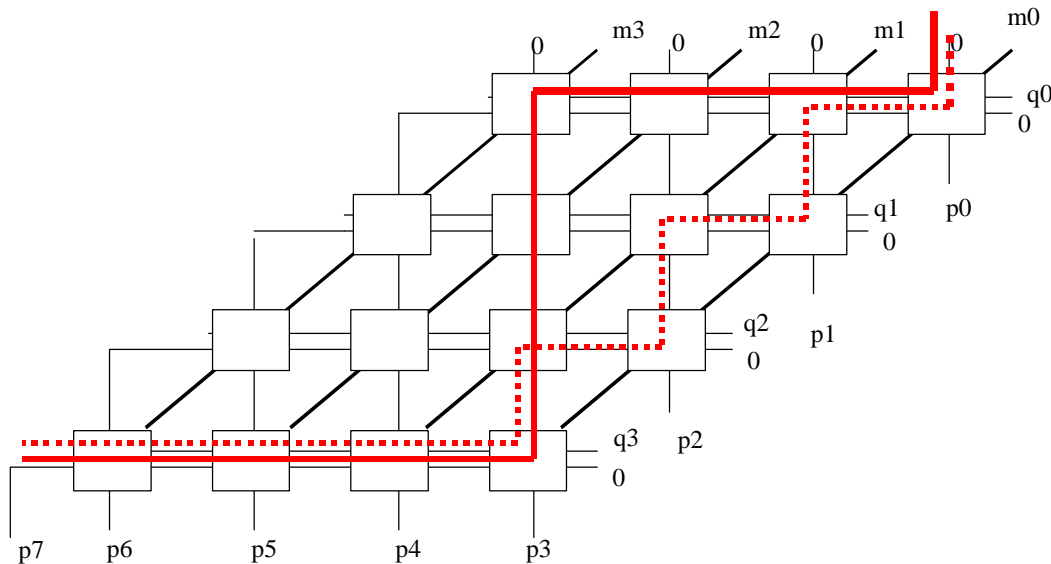All other paths are identical to one of the two essential ones.



Worst case propagation delay: 16.4 ns